

Digital Integrated Circuit Design
CMPE 530/630

Combinational Circuit Design


Dr. Cory Merkel



Learning Objectives

- » Discuss the pros and cons of different combinational circuit design approaches and logic families
- » Be able to estimate and compare the logical effort, parasitic delay, and overall delay of different design approaches
- » Identify some of the common pitfalls encountered by designers when designing combinational circuits

Logic Styles/Families

 

Primary focus in this course.

Complementary/Static CMOS


» Pros

- Good noise margins
- Fast
- Low power
- Good variation tolerance
- Easy to design
- Most widely-used style for combinational logic

» Cons

- Not always the fastest or most area-efficient

 » There are a few ways we can optimize static CMOS circuits



Complementary/Static CMOS






» Bubble pushing

- Idea: Convert AND-OR logic to NAND-NOR logic using DeMorgan's Law
 - Reduces transistor count

» $\overline{AB} = \overline{A} + \overline{B}$

» $\overline{A + B} = \overline{A} \overline{B}$

     » Consider the logic function $Y = AB + CD$:




(a) Has 18
transistors

(d) Has 12
transistors

Complementary/Static CMOS

» Compound gates

 
- Instead of using multiple NAND/NOR/Inverter gates, we can combine a complex logic function into a single gate
- Whereas NAND and NOR have the same logical effort for every input, compound gates can have different logical efforts for each input:



Complementary/Static CMOS


- » Which is faster? Network of NAND/NOR or compound gate?
- » $Y = AB + CD$
 - Assume each input has 20 units of capacitance and the output drives 100 units of capacitance

NAND/NOR

 

$$\begin{aligned}
 H &= \frac{100}{20} = 5 \\
 B &= 1 \\
 G &= \frac{4}{3} \times \frac{4}{3} = \frac{16}{9} \\
 P &= 2 + 2 = 4 \\
 F &= GBH = \frac{80}{9} \\
 \hat{f} &= F^{1/N} = 3 \\
 D &= N\hat{f} + P = 10 \\
 C_{in2} &= \frac{C_{out2} \times g_2}{\hat{f}} = \frac{100 \times 4/3}{3} = 44
 \end{aligned}$$

Compound

 

$$\begin{aligned}
 H &= \frac{100}{20} = 5 \\
 B &= 1 \\
 G &= \frac{6}{3} \times 1 = 2 \\
 P &= 12/3 + 1 = 5 \\
 F &= GBH = 10 \\
 \hat{f} &= F^{1/N} = 3.2 \\
 D &= N\hat{f} + P = 11.3 \\
 C_{in2} &= \frac{C_{out2} \times g_2}{\hat{f}} = \frac{100 \times 4/3}{3} = 31
 \end{aligned}$$

Compound gates
aren't necessarily
fastest!

Complementary/Static CMOS

» Gate input ordering


- Different inputs/transitions have different logical efforts and parasitic delays associated with them
- Even simple gates like NAND have slight differences in g and p for different inputs:

» Case 1: $A = 1, B: 0 \rightarrow 1$

- Node x is initially at $V_{dd} - V_{tn}$
- $t_{pf} = \left(\frac{R}{2}\right) 2C + R(6C) = 2.33\tau$

» Case 2: $B = 1, A: 0 \rightarrow 1$

 - Node x is initially at 0
- $t_{pf} = R(6C) = 2\tau$



Complementary/Static CMOS

- » Logical effort and parasitic delay of NAND gates in IBM 65 nm process:
 - Found by extracting slope and intercept of $d = gh + p$

# of inputs	Input	Rising Logical Effort g_u	Falling Logical Effort g_d	Average Logical Effort g	Rising Parasitic Delay p_u	Falling Parasitic Delay p_d	Average Parasitic Delay p
2	<i>A</i>	1.40	1.12	1.26	2.46	2.48	2.47
	<i>B</i>	1.31	1.16	1.24	1.97	1.82	1.89
3	<i>A</i>	1.76	1.27	1.51	4.77	4.10	4.44
	<i>B</i>	1.73	1.32	1.52	3.93	3.60	3.77
	<i>C</i>	1.59	1.38	1.48	3.05	2.43	2.74
4	<i>A</i>	2.15	1.42	1.78	7.63	5.94	6.79
	<i>B</i>	2.09	1.48	1.78	6.67	5.37	6.02
	<i>C</i>	2.08	1.53	1.80	5.32	4.51	4.91
	<i>D</i>	1.90	1.59	1.75	4.04	2.93	3.49

- » *Outer input* – Closer to supply rail
- » *Inner input* – Closer to output
- » Parasitic delay is lowest when inner input switches last
- » Signals that arrive 'late' should be connected to inner inputs to minimize delay



Complementary/Static CMOS

» Asymmetric gates

- Idea:
 - 1.) Connect critical input(s) to inner input
 - 2.) In series networks, reduce width of critical input to reduce logical effort
 - 3.) Increase width of other transistors in series to maintain overall resistance
 - 4.) Reduce width of non-critical parallel transistors to reduce parasitic capacitance

» Example:

  - Logical effort is $10/9$ for A , which is better than the typical NAND g of $4/3$
- Reset input logical effort is higher ($5/3$)






Complementary/Static CMOS

» Skewed gates

- Used when one *transition* (rising or falling) is more important than the other
- HI-skew – Favors rising output
 - Decrease size of PDN transistors
- LO-skew – Favors falling output
 - Decrease size of PUN transistors
- Degree of skewing = β_f / β_s , where β_f and β_s are the fast and slow transitions, respectively
- Noise margin are affected

» Example:

   

Logical effort for
rising transition:

$$g_u = \frac{2.5}{3} = 5/6$$


Logical effort for
falling transition:

$$g_d = \frac{2.5}{1.5} = 5/3$$


Complementary/Static CMOS

» More examples of skewed gates:








Unskewed

 

HI-skew

 


LO-skew

      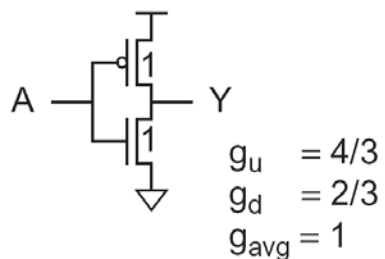




Complementary/Static CMOS

- » What is the best ratio of P and N sizes?
 - So far we have chosen based on equal rise/fall delay
- » We could optimize by choosing based on best *average* delay
- » Delay of FO1 inverter:
 - $\mu \equiv \mu_n / \mu_p$
 - $t_{pdf} = (P + 1)$
 - $t_{pdr} = (P + 1)(\mu / P)$
 - $t_{pd} = (P + 1)(1 + \mu / P) / 2 = (P + 1 + \mu + \mu / P) / 2$
 - $dt_{pd} / dP = (1 - \mu / P^2) / 2 = 0$
 - Least average delay for $P = \sqrt{\mu}$
- » Delay not affected much, but power and area are significantly reduced
- » Cons: Noise margins, asymmetric transitions

 

Complementary/Static CMOS

» CMOS gates with optimal P/N ratio:

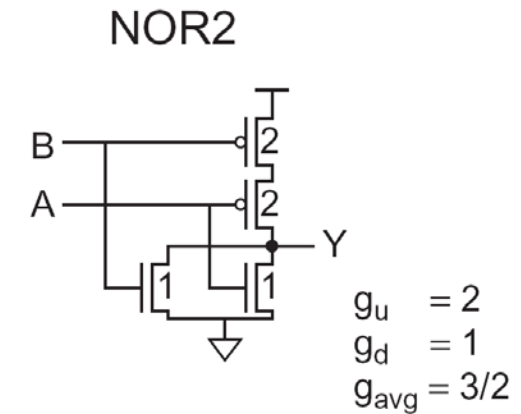  




» NOR structures affected more

Ratioed Circuits

» NMOS logic

- Primary approach in 70's and 80's before CMOS matured
- Static load → Constant static power consumption for high output
 - PUN/PDN ratio must be carefully set for proper rise/fall times, noise margins, etc.
- CMOS eventually displaced NMOS logic due to high static power consumption

   » (a) and (c) use components exacerbated by body effect



Ratioed Circuit

» Pseudo-nMOS





- Motivation, remove large PMOS transistors in PUN to reduce delay/power

» Use grounded PMOS as load

- Size affects speed, noise margins, power

» Best size is process-dependent

    
- Usually $\sim 1/3$ - $1/6$ of minimum NMOS size




Ratioed Circuits

» Pseudo-nMOS gates:

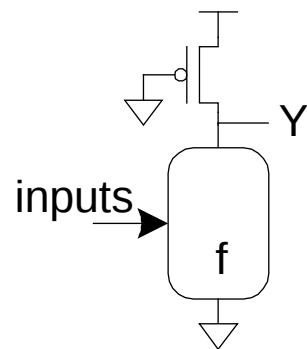- PMOS sizes are selected to be about $\frac{1}{4}$ strength of NMOS
- PMOS produces current of $I/3$, NMOS produces $4I/3$




Inverter

 


$$\begin{aligned}g_u &= 4/3 \\g_d &= 4/9 \\g_{avg} &= 8/9 \\p_u &= 6/3 \\p_d &= 6/9 \\p_{avg} &= 12/9\end{aligned}$$

NAND2

 

$$\begin{aligned}g_u &= 8/3 \\g_d &= 8/9 \\g_{avg} &= 16/9 \\p_u &= 10/3 \\p_d &= 10/9 \\p_{avg} &= 20/9\end{aligned}$$

NOR2

 


$$\begin{aligned}g_u &= 4/3 \\g_d &= 4/9 \\g_{avg} &= 8/9 \\p_u &= 10/3 \\p_d &= 10/9 \\p_{avg} &= 20/9\end{aligned}$$

- » Remember, logical effort and parasitic delay are ratios of input/parasitic capacitance to those of a unit inverter that can provide the same output current
- » Pseudo-nMOS is slower for NAND structures and faster for NOR structures


Cascode Voltage Switch Logic

» CVSL

 
- Advantage of ratioed logic without static power consumption



(a)

 

(b)

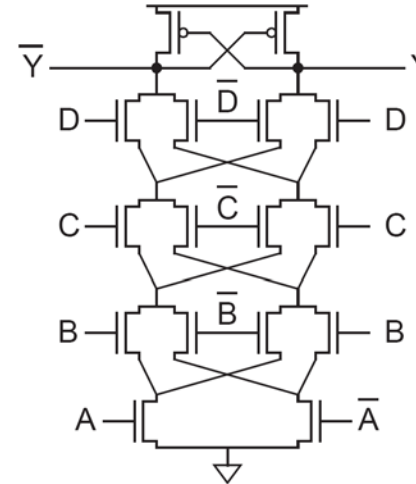

(c)

» Disadvantages:

- Need true and complement of all inputs
- Still usually slower than static CMOS

Dynamic Logic

- » Idea: Advantage of ratioed logic (i.e. reduced input cap. from PMOS) without:
 - Contention during falling transition
 - Slow rise times due to high PUN resistance

» Accomplished by clocking the PUN:


1.) Precharge phase:

- $\phi = 0$
- Output charges to V_{dd}

2.) Evaluate phase:

- $\phi = 1$
- Output remains or falls depending on inputs


» Fastest commonly-used circuit family

 

Footer transistor added when input can't be guaranteed to be 0 during pre-charge.

Dynamic Logic

 - » Precharge transistor is sized for $2 \times R$
 - Reduces capacitive load on clock
 - Reduces parasitic delay
- » Reduced logical effort and parasitic delay compared to static CMOS and ratioed logic because:
 - Smaller PUN **AND** no contention during transition




Dynamic Logic

» Monotonicity problem

- During evaluation, the inputs to a dynamic logic gate must be *monotonically rising*
 - $0 \rightarrow 0$, $0 \rightarrow 1$, $1 \rightarrow 1$ are ok, $1 \rightarrow 0$ is not!



» Example:

 - Dynamic logic inverter violating monotonicity:




Dynamic Logic

  - » Monotonicity can be violated when domino gates are connected
- » Example:
 - This dynamic logic buffer will not work correctly






Domino Logic

 - » Domino logic solves the monotonicity problem by forcing every gate output to be monotonically rising
 - Achieved by adding a static CMOS inverter
- » Inverter is usually HI-skew since rising transition is most important
 - Falling transition of a series of gates occurs in parallel, while the rising transition occurs sequentially



Domino Logic

» Example:

   

» During pre-charge, outputs are set up like dominos, and then fall, one-by-one

Domino Logic

- » Notice that domino logic can only implement non-inverting functions
 - e.g. AND, OR, buffer
- » We can't directly implement inverting functions with domino logic
 - e.g. NAND, NOR, XOR, NOT
- » Three techniques to overcome this:
 - Use static logic for inverting sub-functions
 - Directly cascade gates without CMOS inverter and delay clock to later stages
 - Use dual-rail domino logic


Dual-Rail Domino Logic

» Similar to CVSL


- Instead of cross-coupled PMOS, they are connected to clock

sig_h	sig_l	Meaning
0	0	Precharged
0	1	'0'
1	0	'1'
1	1	Invalid

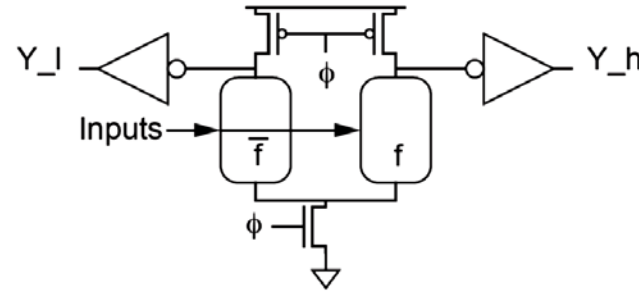
- ## » NAND gate can be connected to outputs to detect end of computation



(a)

 

(b)

 

(c)


Dynamic Logic – Charge Keepers

» Due to leakage and/or noise, charge may leak from the dynamic node of a dynamic logic gate:

- The dynamic node may fall to '0' even if the inputs would normally keep it at '1'

» One solution is to add a 'charge keeper'


 
- Keeps charge on dynamic node unless inputs cause it to discharge



Dynamic Logic – Charge Keepers

» Charge keepers need to be sized carefully

 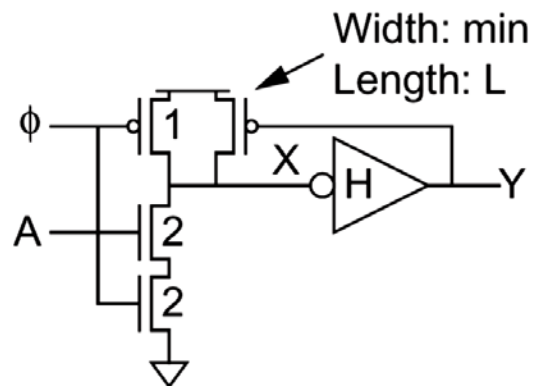- Too strong
 - Large contention current, output may not be able to switch
- Too weak
 - Can't counteract effect of leakage/noise
- Generally, should be weaker than minimally-sized transistor
 - Minimum width, increased length




Dynamic Logic – Charge Sharing

» Consider the dynamic NAND gate below, where

- Initially node x is 0, A=B=0, Y is precharged
- During evaluation, A=1, B=0
 - Charge will move from capacitor C_y to C_x until their voltage is the same:

$$V_x = V_y = \frac{C_y}{C_x + C_y} V_{dd}$$

 
If $C_x \gg C_y$, then V_y may fall below a legal '1' value.



Dynamic Logic – Charge Sharing

» Solutions

 - Make sure that inputs are high during precharge
 - May require a lot of logit
- Add 'secondary' precharge transistors to ensure all internal nodes are charged:



» Adverse effect:

- Falling transition becomes slower because more charge has to be discharged to ground

Multiple Output Domino Logic

» Consider the functions

$$\begin{aligned}c_1 &= g_1 + p_1 c_0 \\c_2 &= g_2 + p_2 (g_1 + p_1 c_0) \\c_3 &= g_3 + p_3 (g_2 + p_2 (g_1 + p_1 c_0)) \\c_4 &= g_4 + p_4 (g_3 + p_3 (g_2 + p_2 (g_1 + p_1 c_0)))\end{aligned}$$


» Some functions contain “subfunctions”

- e.g. $g_1 + p_1 c_0$ is a subfunction that occurs in all of them


» Can we re-use subfunctions to reduce area/power?

Multiple Output Domino Logic

One domino gate for each function:

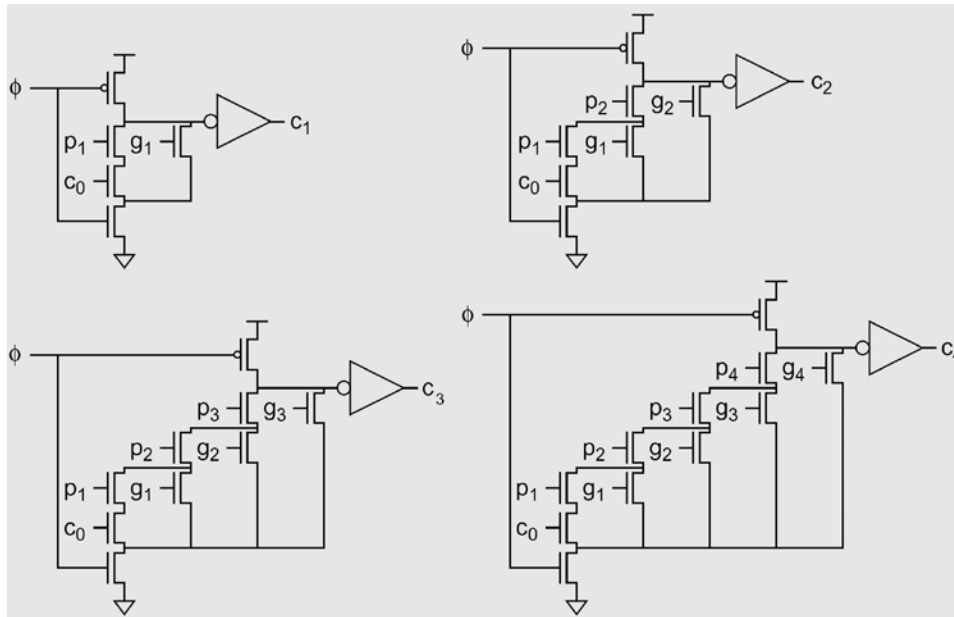


Multiple output domino logic:

 

- » Precharge transistor for each subfunction
- » “Sneak paths” can occur for some input combinations
 - Need to make some inputs mutually exclusive to avoid

Multiple Output Domino Logic


» Sneak path example:

 


» The two '1' inputs should be mutually exclusive to avoid the sneak path

Different Circuit Family Implementations of 2-input MUXes


Static CMOS

 


Pseudo-nMOS

 


CVSL

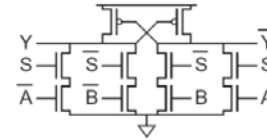


Domino

 


Dual-Rail Domino

 


CPL

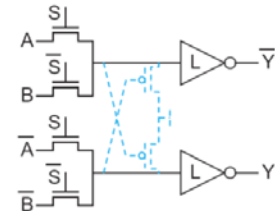


EEPL

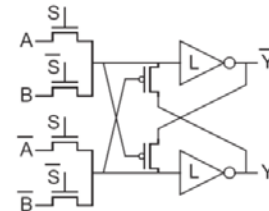


DCVSPG

 


SRPL

 


PPL

 

DPL

 

CMOSTG

 

LEAP

