 


Recap: RC Delay Model



- Idea: ⁽¹⁾ estimate each transistor as



- (2) Draw equivalent ^{RC} circuit for t_{pr} , t_{pf} , t_{er} , t_{ef} delays.

- (3) $t = \sum \sum R_i C_i$ where R_i is a resistor on the path from source to C_i



Example: $y = AB + C$, $M_n = 2M_p$

  

So, minimum width = 4λ

Find t_{er} when output drives A input of h identical gates


Best Case)

 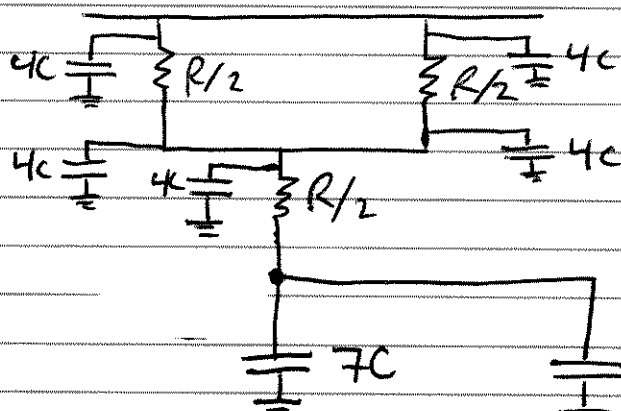

$$t_{er} = \left(\frac{R}{4}\right) 12C + \left(\frac{R}{4} + \frac{R}{2}\right) (7+6h)C = \boxed{\frac{3RC+21}{4} RC + \frac{9}{2} hRC}$$

Find t_{pr} when output drives n identical gates

Worst-case)

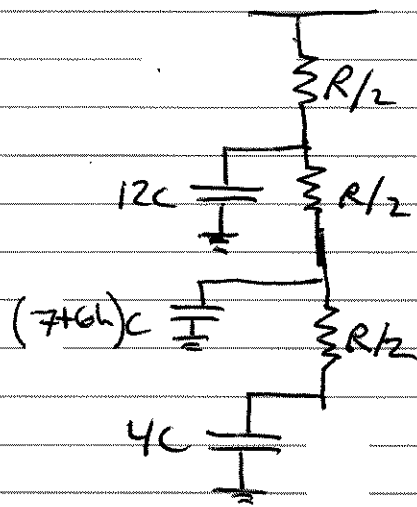


$$t_{pr} = \frac{R}{2}(12C) + \left(\frac{R}{2} + \frac{R}{2}\right)(7+6h)C + (R/2 + R/2)4C$$

$$= 6RC + 7RC + 6hRC + 4RC$$

$$t_{pr} = (17+6h)RC$$

 Let $\tau' =$ the parasitic delay of the unit inverter (not driving any load)



$$\rightarrow \tau' = 3RC$$

Then,
$$d \equiv \frac{t}{\tau} = f + p = gh + p$$

$f =$ "effort delay"

$g =$ "logical effort" - ratio of gate input ^{cap.} to unit inverter

$h =$ "electrical effort" or fanout $\rightarrow h = \frac{C_{out}}{C_{in}}$

$p =$ "parasitic delay" - delay when no load is attached

for our AOI t_{pr} :


$$d = 2h + \frac{17}{3}$$

$\nwarrow$ logical effort $\nwarrow$ fanout $\nwarrow$ parasitic delay

Notice d is linear function of $h \rightarrow$ linear delay model

Logical effort and parasitic delay


example: n -input NAND Gate

 

$$g = \frac{n+2}{3}$$

$$p = n$$

n-input NOR gate:

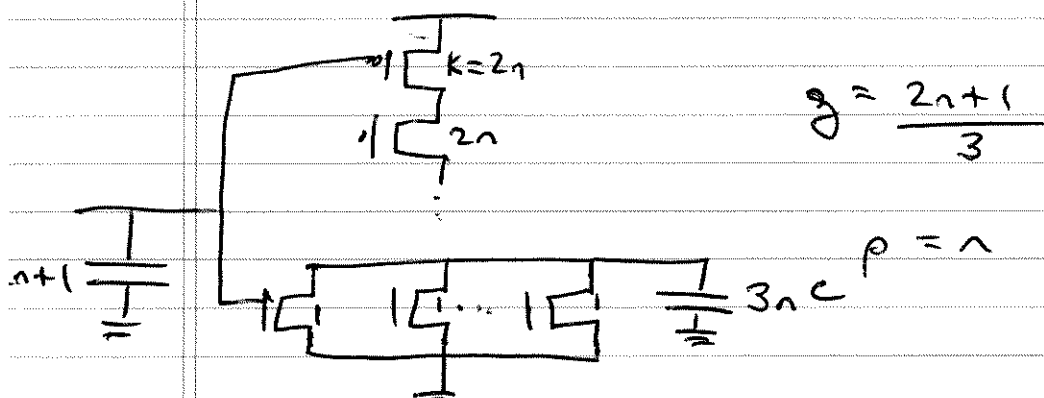


★ NOR gates are $\approx 2\times$ slower than NAND gates

• What was wrong with our parasitic delay estimation?

- need to include internal capacitances...

 Example n-input NAND where all inputs are 1 except bottom, which then rises...




$$t_{par} = 3nRC + \sum_{i=1}^{n-1} \left(\frac{iR}{n} \right) (nC)$$

$$= \left(\frac{n^2}{2} + \frac{5n}{2} \right) RC$$

$$\text{or } p = \frac{n^2 + 5n}{2}$$

★ Actually quadratic in n , not linear $\rightarrow$ split big gates into small ones

F04 delays

 

$$t_p = 15RC, \alpha = 5$$

- ★ F04 delays are roughly $\frac{1}{3}$ to $\frac{1}{2}$ of drawn channel length in picoseconds
for TSMC 180nm - $F04 \approx 60-90$ ps

Drive

- Redefine unit inverter to have input capacitance of 1

$$x = \frac{C_{in}}{f} \quad \} \text{ drive of a gate}$$


or

$$d = \frac{C_{out}}{x} + p$$


Class exercise

- Calculate the rising propagation delay of $(A+B)(C+D)$ w/ fanout of h .
- What is the logical effort?
- What is the parasitic delay?
- What is the drive if minimum sizing is used?

 Assume $W_{min} = 4\lambda$, $\mu_n = 2\mu_p$



$$8 + 8 + 12 = 28C + G_{ch}$$

 


Worst-case: $A=1, B=0, C=0, D=0$

$$t_{pr} = \frac{R}{2}(8C) + R(28C + G_{ch}) = 6hRC + 32RC$$

- logical effort = $\frac{6}{3} = 2$
- parasitic delay = $\frac{32}{3}$
- drive = $\frac{C_{in}}{3g} = \frac{2}{3(2)} = \frac{1}{3}$

Delay in Multi-stage Networks

 


$$g_1 = 1 \quad g_2 = 5/3 \quad g_3 = 4/3 \quad g_4 = 1$$

$$h_1 = x/i \quad h_2 = y/x \quad h_3 = z/y \quad h_4 = z/z$$

Definitions: ^{logical} Path effort $\rightarrow G \equiv \prod g_i$

Path electrical effort $\rightarrow H \equiv \frac{C_{out}(path)}{C_{in}(path)}$

 Path effort $\rightarrow F \equiv \prod f_i = \prod g_i h_i$



$$G = 1 \times 1 = 1$$

$$H = \frac{90}{5} = 18$$

$$F = \left(1 \times \frac{30}{5}\right) \left(1 \times \frac{90}{15}\right) = 36 \neq GH!$$

Branching effort $\rightarrow b \equiv \frac{C_{onpath} + C_{offpath}}{C_{onpath}}$

Path branching effort $\rightarrow B \equiv \prod b_i$

$$\boxed{F = GBH}$$

Path Delay $\rightarrow D \equiv \sum d_i = D_F + P$

$D_F \equiv \sum f_i \rightarrow$ Path effort delay

$P \equiv \sum p_i \rightarrow$ Path parasitic delay


Path effort delay is minimized when $f_i = f_j \forall i, j$
 or, $\hat{f} = F^{1/N}$

Minimum possible delay of N -stage path is

$$D = NF^{1/N} + P$$

Capacitance transformation formula:
 
$$C_{in_i} = \frac{C_{out_i} \times g_i}{\hat{f}} \quad \left. \vphantom{\frac{C_{out_i} \times g_i}{\hat{f}}} \right\} \begin{array}{l} \text{Best input capacitance} \\ \text{for a gate given its} \\ \text{output capacitance} \end{array}$$



$$G = \left(\frac{4}{3}\right) \left(\frac{5}{3}\right) \left(\frac{5}{3}\right) = 100/27$$

$$H = 45/8$$

$$B = \left(\frac{3x}{x}\right) \left(\frac{2y}{y}\right) = 6$$

$$F = GBH = 125$$

Best stage effort is $\hat{f} = 125^{1/3} = 5$

$$P = 2 + 3 + 2 = 7$$


$$D = N\hat{f} + P = 3 \times 5 + 7 = 22 \text{ or } 4.4 \text{ FO4 delays}$$

Now find input capacitance

$$y = C_{in3} = \frac{45(5/3)}{5} = 15$$

$$x = C_{in2} = (15 + 15) \times (5/3) / 5 = 10$$

 So, we can size transistors according to C_{in} and constraint of equal rise/fall times
What's the best # of Stages?



n_1 stages
path effort F

$$D = NF^{1/N} + \sum_{i=1}^{n_1} p_i + (N - n_1)p_{inv}$$

Let $p = F^{1/N}$

$$\frac{\partial D}{\partial N} = 0 \rightarrow p_{inv} + p(1 - \ln p) = 0$$

$$p = 2.71828 (e) \text{ with } p_{inv} \approx 0$$

$$\text{or } p = 3.59 \text{ with } p_{inv} = 1$$

So, a path has least delay when

$$N = \log_p F$$