

Digital Integrated Circuit Design
CMPE 530/630

Memory

Dr. Cory Merkel




Learning Objectives

- » Understand basic architectures and circuit designs for common memories.

Outline


- » Memory Arrays
- » SRAM Architecture
 - SRAM Cell
 - Decoders
 - Column Circuitry
 - Multiple Ports
- » Serial Access Memories

Memory Arrays

 



Array Architecture

 - » 2^n words of 2^m bits each
- » If $n \gg m$, fold by 2^k into fewer rows of more columns
- » Good regularity – easy to design
- » Very high density if good cells are used




12T SRAM Cell

  - » Basic building block: SRAM Cell
 - Holds one bit of information, like a latch
 - Must be read and written
- » 12-transistor (12T) SRAM cell
 - Use a simple latch connected to bitline
 - $46 \times 75 \lambda$ unit cell





6T SRAM Cell

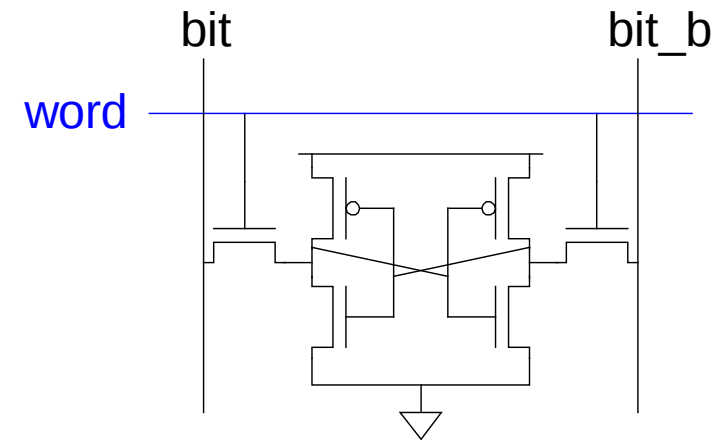- » Cell size accounts for most of array size
 - Reduce cell size at expense of complexity
- » 6T SRAM Cell
 - Used in most commercial chips
 - Data stored in cross-coupled inverters
- » Read:
 - Precharge bit, bit_b
 - Raise wordline
- » Write:
 - Drive data onto bit, bit_b
 - Raise wordline





SRAM Read

  - » Precharge both bitlines high
- » Then turn on wordline
- » One of the two bitlines will be pulled down by the cell
- » Ex: $A = 0, A_b = 1$
 - bit discharges, bit_b stays high
 - But A bumps up slightly
- » *Read stability*
 - A must not flip
 - $N_1 \gg N_2$




SRAM Write

  - » Drive one bitline high, the other low
- » Then turn on wordline
- » Bitlines overpower cell with new value
- » Ex: $A = 0$, $A_b = 1$, $\text{bit} = 1$, $\text{bit}_b = 0$
 - Force A_b low, then A rises high
- » *Writability*
 - Must overpower feedback inverter
 - $N2 \gg P1$




SRAM Sizing

 - » High bitlines must not overpower inverters during reads
- » But low bitlines must write new value into cell




SRAM Column Example

Read

 


Write

 


Static Noise Margins

 - » Static noise margins (SNM) define the amount of noise the SRAM cell can withstand
- » Hold margin
 - SNM is the width of the largest square that can be fit between the two inverter voltage transfer characteristics curves (a.k.a. butterfly diagram)




 
- If inverters are not identical, use smaller of the two squares
- Hold margin increases with V_{dd} , V_{th} , inverter gain




Static Noise Margins

» Read margin

 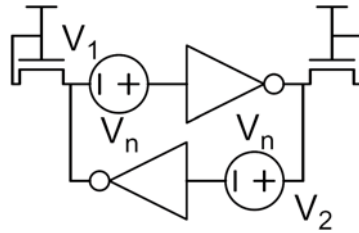- Minimum voltages on butterfly diagram are >0 due to voltage on bitlines:




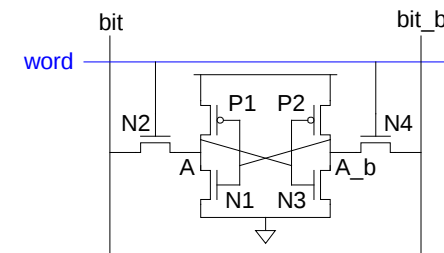
- Read margin increases with relative strength of pulldown to access transistor, or *cell ratio*: W_{N1}/W_{N2}
- Also increases with V_{dd} , V_{th} , and reducing wordline voltage relative to V_{dd}



Static Noise Margins

» Write margin


 
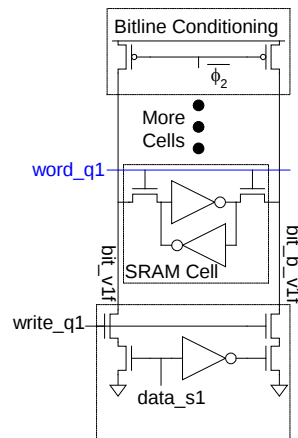
- *Smallest* square that can be drawn between curves in butterfly diagram



- Write margin increases with increased access transistor strength, weaker pullup transistor, increased wordline voltage
 - In contrast to read margin


SRAM Layout

   - » Cell size is critical: $26 \times 45 \lambda$ (even smaller in industry)
- » Tile cells sharing V_{DD} , GND, bitline contacts



Thin Cell

 
- » In nanometer CMOS
 - Avoid bends in polysilicon and diffusion
 - Orient all transistors in one direction
- » *Lithographically friendly or thin cell* layout fixes this
 - Also reduces length and capacitance of bitlines



Commercial SRAMs

» Five generations of Intel SRAM cell micrographs


 
- Transition to thin cell at 65 nm
- Steady scaling of cell area





Decoders

- » $n:2^n$ decoder consists of 2^n n -input AND gates
 - One needed for each row of memory
 - Build AND from NAND or NOR gates
 - Lower logical effort $\rightarrow$ Reduced delay

Static CMOS

  


Pseudo-nMOS

  

Decoder Layout

 - » Decoders must be pitch-matched to SRAM cell
 - Requires very skinny gates



Large Decoders


- » For $n > 4$, NAND gates become slow
 - Break large gates into multiple smaller gates
- » Delay of inverter $\rightarrow$ 4-input NAND

$$\begin{aligned}
 D &= d_{INV} + d_{NAND4} \\
 &= g_{INV}h_{INV} + p_{INV} + g_{NAND4}h_{NAND4} + p_{NAND4} \\
 &\quad 1\left(\frac{6}{3} \times 2^{n-1}\right) + 1 + \left(\frac{6}{3}\right)\left(\frac{C_{word}}{6}\right) + \frac{12}{3}
 \end{aligned}$$

- » Delay of inverter $\rightarrow$ 2-input NAND $\rightarrow$ 2-input NOR

$$\begin{aligned}
 D &= d_{INV} + d_{NAND4} \\
 &= g_{INV}h_{INV} + p_{INV} + g_{NAND2}h_{NAND2} + p_{NAND2} \\
 &\quad + g_{NOR2}h_{NOR2} + p_{NOR2} \\
 &\quad 1\left(\frac{4}{3} \times 2^{n-1}\right) + 1 + \left(\frac{4}{3}\right)\left(\frac{5}{4}\right) + \frac{6}{3} + \left(\frac{5}{3}\right)\left(\frac{C_{word}}{5}\right) + \frac{6}{3}
 \end{aligned}$$

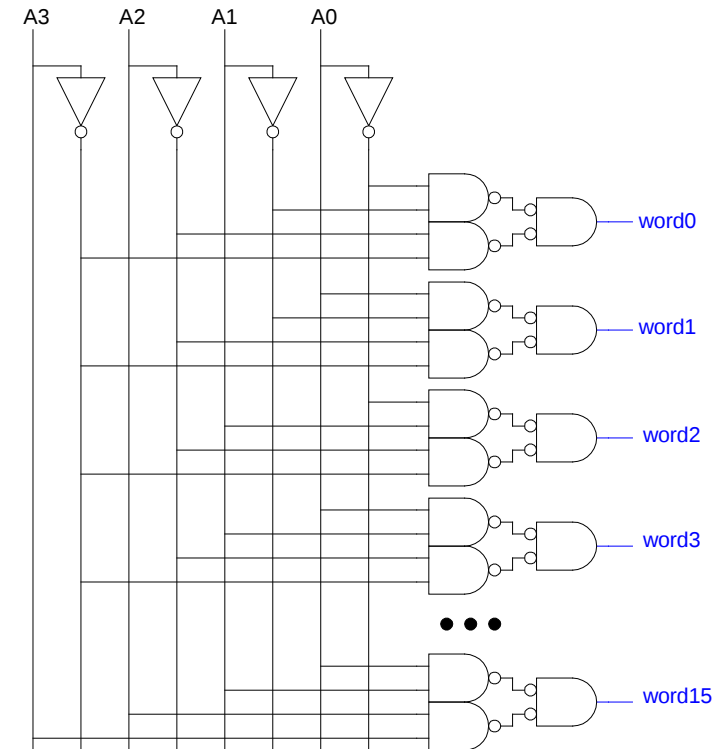
- » For large n , 2-input NAND implementation is $\approx 1.5 \times$ faster...



Predecoding

» Many of these gates are redundant

 - Factor out common gates into predecoder
- Saves area
- Same path effort




Column Circuitry


- » Some circuitry is required for each column
 - Bitline conditioning
 - Sense amplifiers
 - Column multiplexing

Bitline Conditioning

- » Precharge bitlines high before reads

 


 - » Equalize bitlines to minimize voltage difference when using sense amplifiers




Sense Amplifiers

- » One approach is to use high-skew inverters
 - **Large signal approach** → Bitlines have full voltage swing
- » Bitlines have many cells attached
 - Ex: 32-kbit SRAM has 128 rows x 256 cols
 - 128 cells on each bitline
- » $t_{pd} \propto (C/I) \Delta V$
 - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
 - Discharged slowly through small transistors (small I)
- » *Sense amplifiers*
 - Triggered on small voltage swing (reduce ΔV)
 - **Small signal approach**

 


Differential Pair Amp

 - » Differential pair requires no clock
- » But always dissipates static power




Clocked Sense Amp

 - » Clocked sense amp saves power
- » Requires sense_clk after enough bitline swing
- » Isolation transistors cut off large bitline capacitance



Twisted Bitlines

 - » Sense amplifiers also amplify noise
 - Coupling noise is severe in modern processes
 - Try to couple equally onto bit and bit_b
 - Done by *twisting* bitlines




Column Multiplexing

- » Recall that array may be folded for good aspect ratio
- » Ex: 2 kword x 16 folded into 256 rows x 128 columns
 - Must select 16 output bits from the 128 columns
 - Requires 16 8:1 column multiplexers


Tree Decoder Mux

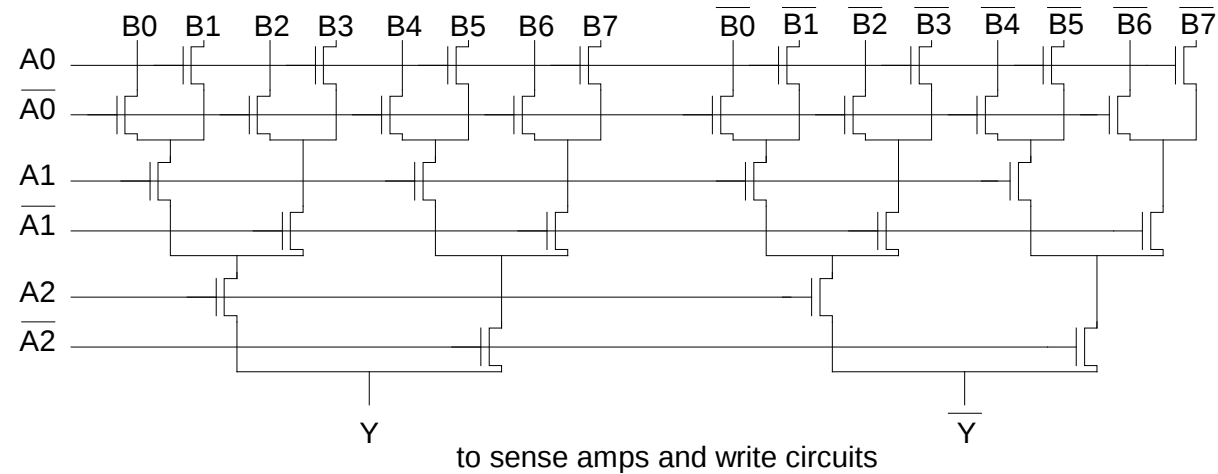- » Column mux can use pass transistors
 - Use nMOS only, precharge outputs
- » One design is to use k series transistors for $2^k:1$ mux
 - No external decoder logic needed




Single Pass-Gate Mux

 - » Or eliminate series transistors with separate decoder



Ex: 2-way Muxed SRAM

 


Multiple Ports

- » We have considered single-ported SRAM
 - One read or one write on each cycle
- » *Multiported* SRAM are needed for register files
- » Examples:
 - Multicycle MIPS must read two sources or write a result on some cycles
 - Pipelined MIPS must read two sources and write a third result each cycle
 - Superscalar MIPS must read and write many sources and results each cycle

Dual-Ported SRAM

» Simple dual-ported SRAM

 - Two independent single-ended reads
- Or one differential write




» Do two reads and one write by time multiplexing

- Read during ph1, write during ph2


Multi-Ported SRAM

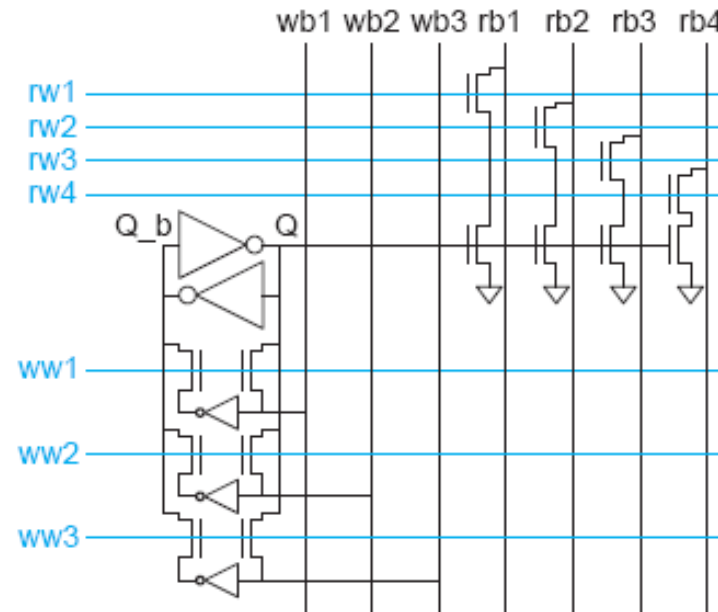- » Adding more access transistors hurts read stability
- » Multiported SRAM isolates reads from state node
- » Single-ended bitlines save area



Large SRAMs

- » Large SRAMs are split into subarrays for speed
- » Ex: UltraSparc 512KB cache
 - 4 128 KB subarrays
 - Each have 16 8KB banks
 - 256 rows x 256 cols / bank
 - 60% subarray area efficiency
 - Also space for tags & control

 

[Shin05]