

Digital Integrated Circuit Design
CMPE 530/630

MOSFET Switch Model and Circuits

Dr. Cory Merkel



Learning Objectives

- » Review basic functionality of metal oxide semiconductor field effect transistors (MOSFETs)
 - Differences between p-type MOSFETs (PMOS) and n-type MOSFETs (NMOS)
- » Understand the tradeoffs between pass transistors, transmission gates, and complementary metal oxide semiconductor (CMOS) logic circuits
- » Be able to convert a logic function into a CMOS, pass transistor, or transmission gate logic circuit and vice versa

Why Digital Logic?

» Advantages

- Better noise tolerance
- Higher precision (can be arbitrarily high!)
- Easier detection/correction of errors
- Simpler/more robust circuits

» Disadvantages


- For some functions analog designs are much simpler and much more size, weight, and power (SWaP)-efficient

Representation of Digital Signals

- » Typically, we represent a logical '1' with V_{DD} and a logical '0' with ground
- » We need to give our circuits some “wiggle room”, though:

V_{OH} =High output voltage V_{OL} = Low output voltage NM_H = High noise margin

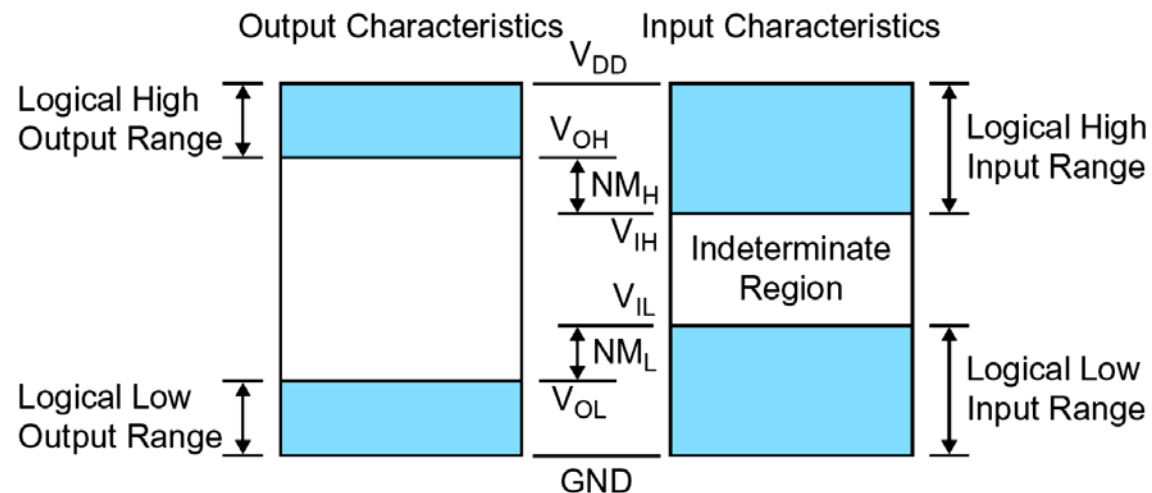V_{IH} = High input voltage V_{IL} = Low input voltage NM_L = Low noise margin






Our Friend, the MOSFET

» Metal Oxide Semiconductor Field Effect Transistor




- We will fully understand this acronym in a couple weeks

» MOSFET Symbols:

NMOS

 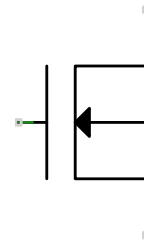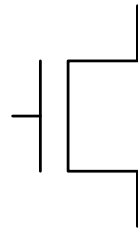


PMOS

   

Our Friend, the MOSFET


» For now, MOSFET = fancy switch

NMOS

 

$g = 0$: Switch OFF
 $g = 1$: Switch ON



PMOS

 



$g = 0$: Switch ON
 $g = 1$: Switch OFF

Our Friend, the MOSFET

 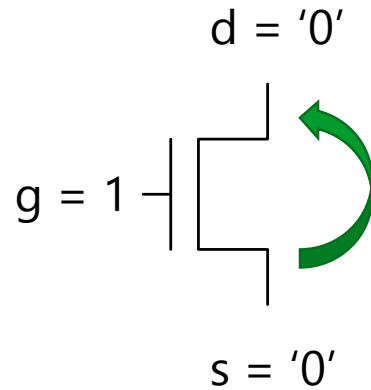» NMOS passes a strong '0' from source to drain and a weak '1' from source to drain:



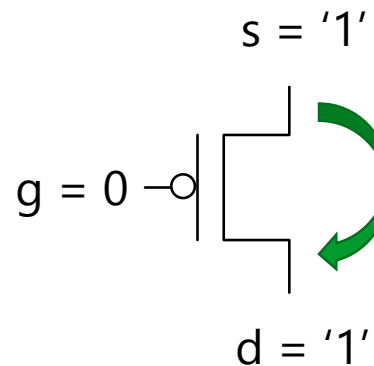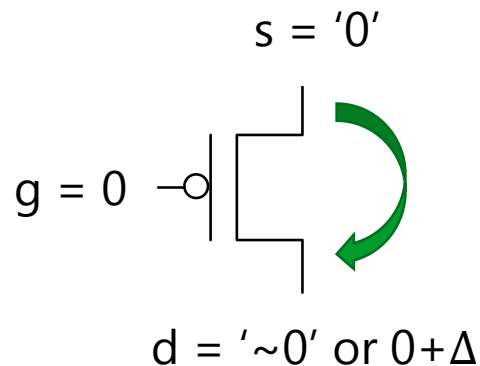
» PMOS passes a strong '1' from source to drain and a weak '0' from source to drain:



Δ is a small value less than 1. We will see exactly what it is later in the course.


Series and Parallel MOSFETs

NMOS

 


A	X	Y
0	0	Z
0	1	Z
1	0	0
1	1	~1

PMOS

 


A	X	Y
0	0	~0
0	1	1
1	0	Z
1	1	Z

Series

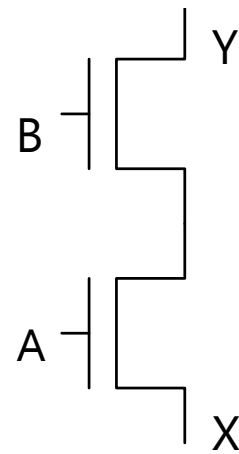


A	B	X	Y
0	0	0	Z
0	0	1	Z
0	1	0	Z
0	1	1	Z
1	0	0	Z
1	0	1	Z
1	1	0	0
1	1	1	~1

 


A	B	X	Y
0	0	0	~0
0	0	1	1
0	1	0	Z
0	1	1	Z
1	0	0	Z
1	0	1	Z
1	1	0	Z
1	1	1	Z

Parallel

 

A	B	X	Y
0	0	0	Z
0	0	1	Z
0	1	0	0
0	1	1	~1
1	0	0	0
1	0	1	~1
1	1	0	0
1	1	1	~1

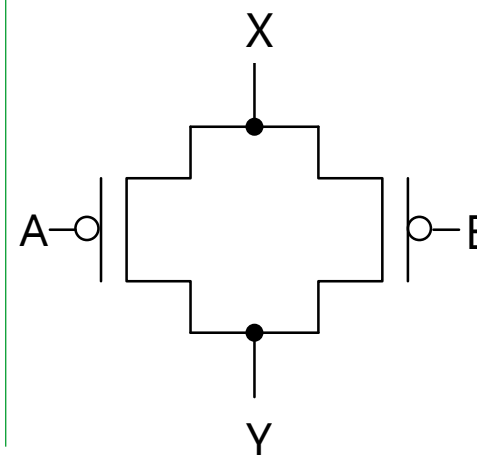

A	B	X	Y
0	0	0	~0
0	0	1	1
0	1	0	~0
0	1	1	1
1	0	0	~0
1	0	1	1
1	1	0	Z
1	1	1	Z

Series and Parallel MOSFETs


» When $X=0$

- Series NMOS behave like NAND
- Parallel NMOS behave like NOR

» When $X=1$

- Series PMOS behave like NOR
- Parallel PMOS behave like NAND


Logic Styles

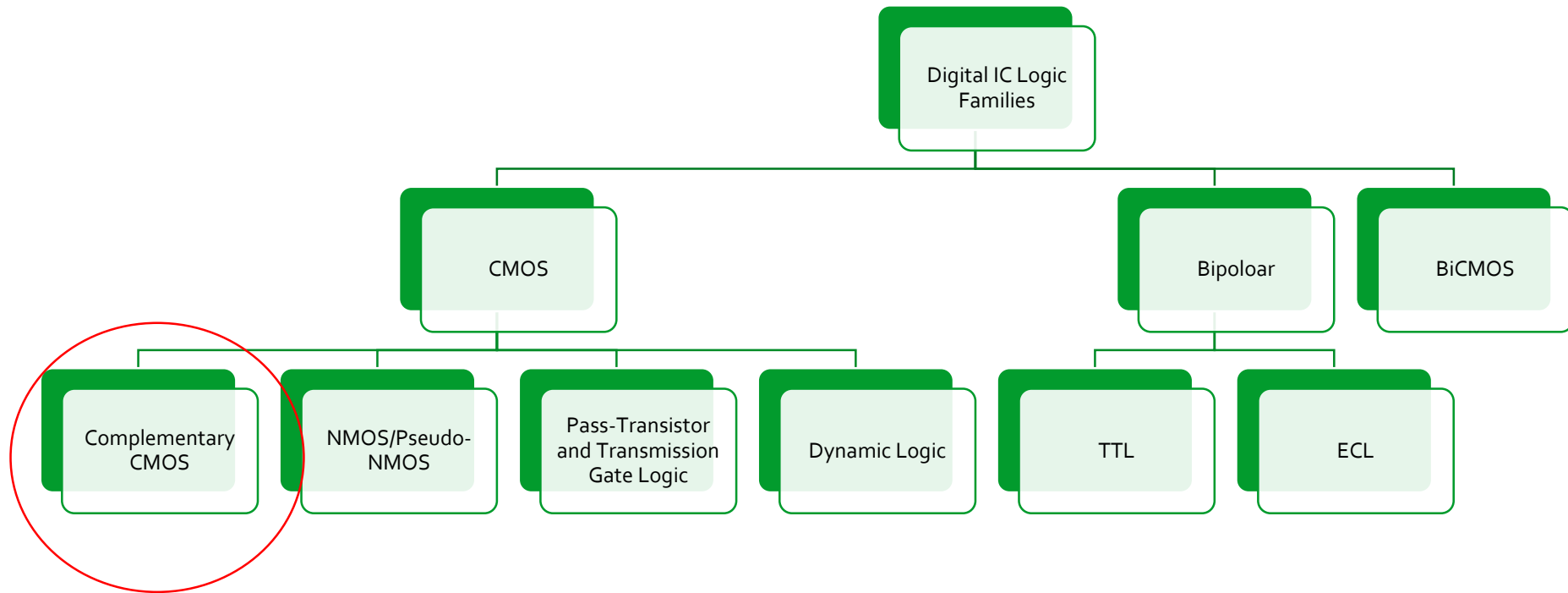

Primary focus in this course.

Design an Inverter Using an NMOS Transistor

» Recall:

 


A	X	Y
0	0	Z
0	1	Z
1	0	0
1	1	~1

We want:

A	Y
0	1
1	0

» Could do this:

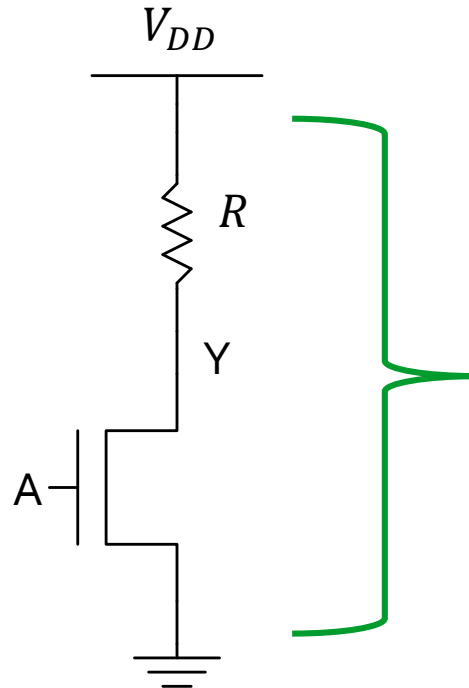

When $A=0$, there is no path to ground, so $Y \approx V_{DD}$ (i.e. '1').


When $A=1$, the switch is closed, so $Y \approx \text{Ground}$ (i.e. '0').

Several issues with this circuit:

- Resistors are large
- High power consumption
- Reduced noise margins
- Slow if R is large

Now Try Using an NMOS and a PMOS Transistor

 
- » When $A=0$, the PMOS is ON and NMOS is OFF
 - Y is “pulled up” to V_{DD}
- » When $A=1$, the NMOS is ON and the PMOS is OFF
 - Y is “pulled down” to ground
- » Power consumption is reduced
 - Why?
- » This is an example of a complementary or static CMOS logic gate



CMOS Logic

» In general, we want:

 
- Output connected to V_{DD} through PMOS transistors – Pull-Up Network (**PUN**)
- Output connected to ground through NMOS – Pull-Down Network (**PDN**)
- Only one supply path (PUN or PDN) on at a time



CMOS Logic

- » How do we make sure only one supply path (PUN or PDN) is on at a time?
- » Easy! Given some logic function Y , we will write it in complemented form (e.g. with a bar over it):


$$Y = \overline{\overline{Y}}$$

 

- » For every **AND** in $\overline{Y}$, there is a **series NMOS** and **parallel PMOS**
- » For every **OR** in $\overline{Y}$ there is a **parallel NMOS** and **series PMOS**

 Example – NAND Gate

- » $Y = \overline{AB} \rightarrow$ Already in complemented form!
- » $\overline{Y} = AB$, so we have a series of NMOS and parallel PMOS:



Example – Compound Logic Gate

» Try these on your own:

- $Y = AB + C$
- $Y = \overline{(A + B)C}$



Symmetric Logic Functions

- » When a logic function is symmetric, complementing its inputs complements its outputs
 - Complementing the inputs leads to complemented outputs
- » In this case, the PUN and PDN are also symmetric or “mirrored”
 - Makes mask design simpler

Pass Transistor Logic

» Pass transistor: Used to pass an *input*, rather than a supply value from input to output

» Examples:

  

» Important: Need a low-impedance path to supply for all possible input combinations!

Differential Pass Transistor Logic

- » Accepts true and complemented inputs
- » Produces true and complemented outputs
- » Eliminates need for inverters

Pass Transistor Logic

» Advantages:


- Reduces number of components compared to complementary CMOS
- Potentially faster due to less capacitance

» Disadvantages

- NMOS passes a weak '1' and PMOS passes a weak '0'
- Can't drive other pass transistor logic circuits
- Noise

Transmission Gates (TG)

 - » Overcome the weak 0/1 issue by using both NMOS and PMOS in parallel:



- » When $A=1$, a strong 1/0 is passed to Y
- » Disadvantage: More transistors

Example: TG MUX

» Try on your own:

- $Y = \bar{S}D_0 + SD_1$

Tri-State Inverter

- » Used when multiple circuits drive a single output
 - Example: Shared bus

