

Digital Integrated Circuit Design  
CMPE 530/630

---

# Power Consumption

Dr. Cory Merkel




## Learning Objectives

- » Be able to describe the primary components of power consumption in CMOS circuits
- » Be able to estimate the power consumption of CMOS gates
- » Be able to discuss how power consumption can be optimized by modifying voltages, frequencies, activity factors, etc.
 
# Evaluating Digital ICs

- » What are the tradeoffs?
- » What influences what?



# What is Power?

- » Power is the rate of work:

$$P(t) \equiv \frac{dW}{dt}$$

- » Voltage is the work per unit charge

$$v(t) \equiv \frac{W}{Q}$$

- » Instantaneous power dissipated by a circuit element is:

$$P(t) = v(t) \frac{dQ}{dt} = v(t)i(t)$$

## Energy and Average Power

» Energy is the time integral of power:

$$E = \int_0^T P(t) dt$$

» Average power is energy over time:

$$P_{avg} = \frac{E}{T} = \frac{1}{T} \int_0^T P(t) dt$$

## Power in Resistors and Capacitors

» Resistors (using Ohm's law):

$$P_R = vi = i^2 R = \frac{v^2}{R}$$

» Capacitors (using  $Q = vC$ ):

$$E_C = \int_0^{\infty} v(t)i(t)dt = \int_0^{\infty} C \frac{dv(t)}{dt} v(t)dt = C \int_0^{V_C} v(t)dv = \frac{1}{2} CV_C^2$$

» Power supplies:

$$P_{V_{dd}}(t) = V_{dd}i_{dd}(t)$$

# Components of Power Consumption

- » Total power consumption is composed of two main components:


$$P_{\text{total}} = P_{\text{dynamic}} + P_{\text{static}}$$

- » Dynamic power is consumed when the circuit is “doing something”
- » Static power is consumed when the circuit is idle
 
# Dynamic Power Consumption

$$P_{dynamic} = P_{switching} + P_{short\ circuit} + P_{glitch}$$

» Dynamic power is primarily caused by gates switching:



$$P_{switching} = \frac{1}{T} \int_0^{\infty} V_{dd} i_{dd}(t) dt = \frac{1}{T} \int_0^{\infty} V_{dd} C \frac{dv_{out}}{dt} dt = \frac{1}{T} C V_{dd} \int_0^{V_{dd}} dv_{out} = \frac{1}{T} C V_{dd}^2$$

# Dynamic Power Consumption

- » Notice that the energy stored by the load capacitor is only half of the total switching energy
  - Half of the energy goes to power dissipation through either the PUN or PDN!
    - “Reversible computing” methodologies seek to reduce or eliminate power consumption by shuffling energy around instead of resupplying it from  $V_{dd}$  or ground
- » Our switching period  $T$  is related to the operating frequency as:  $T = \alpha/f$ , where  $\alpha$  is the “activity factor”:

$$P_{\text{switching}} = \alpha C V_{dd}^2 f$$

- »  $\alpha$  is the probability that a gate will switch from 0 to 1 within  $T$

## Switching Activity Factor

- » Switching activity factor is calculated as:

$$\alpha = \Pr(\text{output} = 0) \Pr(\text{output} = 1) = \bar{P}_Y P_Y = (1 - P_Y) P_Y$$

- » Clocks have  $\alpha = 1$
- »  $\alpha = 0.1$  often used for estimation
- » Exact activity factors requires simulation


| Gate              | $P_Y$                           | $\alpha$ (assuming inputs with $P_Y = 0.5$ ) |
|-------------------|---------------------------------|----------------------------------------------|
| AND <sub>2</sub>  | $P_A P_B$                       | 3/16                                         |
| AND <sub>3</sub>  | $P_A P_B P_C$                   | 7/64                                         |
| OR <sub>2</sub>   | $1 - \bar{P}_A \bar{P}_B$       | 3/16                                         |
| NAND <sub>2</sub> | $1 - P_A P_B$                   | 3/16                                         |
| NOR <sub>2</sub>  | $\bar{P}_A \bar{P}_B$           | 3/16                                         |
| XOR <sub>2</sub>  | $P_A \bar{P}_B + \bar{P}_A P_B$ | 1/4                                          |

## Other Dynamic Power Components


- » During switching, there may be a short period of time that both the PUN and PDN are on
  - Power consumed during this time is called short-circuit power
- » Function of  $V_t/V_{dd}$ 
  - When  $>0.5$ ,  $P_{\text{short circuit}} = 0$
  - Otherwise, typically 2%-10% of switching power
- » Function of input rise/fall times
  - Slower inputs cause higher short circuit power
 
## Other Dynamic Power Components

- » Additional power can be consumed when hazards are present in the circuits, causing “glitches”:



# Inverter Dynamic Power

 

# Methods for Reducing Dynamic Power Consumption

- » Recall most of dynamic power comes from switching:

$$P_{\text{switching}} = \alpha C V_{dd}^2 f$$

- » Reduce  $\alpha$ 
  - Clock/power gating
- » Reduce  $C$ 
  - Smaller transistors, better materials
- » Reduce  $V_{dd}$  and  $f$ 
  - Dynamic voltage/frequency scaling

# Static Power Consumption

- » Static power consumption occurs when circuits are idle

$$P_{static} = (I_{sub} + I_{gate} + I_{junct} + I_{contention})V_{dd}$$

Subthreshold current

Gate tunneling current

Source/drain diffusion leakage

Contention in ratioed circuits

- » Large static power has led to the era of “dark silicon”
  - Large portion of circuit has to be disconnected from supply at any given time to meet power constraints

# Static Power Consumption

## » Subthreshold leakage

- Even when  $V_{gs} < V_{th}$ , current flows due to diffusion

$$I_{sub} = \beta V_T^2 (n - 1) e^{\frac{\overset{\text{DIBL Coefficient}}{V_{eff}} + \overset{\text{Body Effect Coefficient}}{\eta}(V_{ds} - V_{dd}) - k_{\gamma} V_{sb}}{nV_T}} \left(1 - e^{-\frac{V_{ds}}{V_T}}\right)$$

## » Static power reduction techniques

- Transistor stacking
  - Series transistors have less leakage
- Power gating
  - Use transistor to cut off the supply to a particular circuit
- Multiple threshold voltages
  - Use higher threshold in non-critical paths

# Shrinking Transistor Sizes



» Why does the IC industry want to scale?

| Parameter                       | Sensitivity           | Dennard Scaling | Constant Voltage | Lateral Scaling |
|---------------------------------|-----------------------|-----------------|------------------|-----------------|
| L: Length                       |                       | 1/S             | 1/S              | 1/S             |
| W: Width                        |                       | 1/S             | 1/S              | 1               |
| $t_{ox}$ : gate oxide thickness |                       | 1/S             | 1/S              | 1               |
| $V_{DD}$ : supply voltage       |                       | 1/S             | 1                | 1               |
| $V_t$ : threshold voltage       |                       | 1/S             | 1                | 1               |
| NA: substrate doping            |                       | S               | S                | 1               |
| $\beta$                         | $W/(Lt_{ox})$         | S               | S                | S               |
| $I_{on}$ : ON current           | $\beta(V_{DD}-V_t)^2$ | 1/S             | S                | S               |
| R: effective resistance         | $V_{DD}/I_{on}$       | 1               | 1/S              | 1/S             |
| C: gate capacitance             | $WL/t_{ox}$           | 1/S             | 1/S              | 1/S             |
| $\tau$ : gate delay             | RC                    | 1/S             | $1/S^2$          | $1/S^2$         |
| f: clock frequency              | $1/\tau$              | S               | $S^2$            | $S^2$           |
| E: switching energy / gate      | $CV_{DD}^2$           | $1/S^3$         | 1/S              | 1/S             |
| P: switching power / gate       | Ef                    | $1/S^2$         | S                | S               |
| A: area per gate                | WL                    | $1/S^2$         | $1/S^2$          | 1               |
| Switching power density         | P/A                   | 1               | $S^3$            | S               |
| Switching current density       | $I_{on}/A$            | S               | $S^3$            | S               |

Faster, more energy-efficient chips @ lower cost

# Adverse Effects of Scaling

## » Power Consumption

  


Source: ITRS

- » More transistors/chip → More dynamic power
- » As threshold voltages are reduced, transistors become more “leaky”
  - Large static power consumption


 
## Division of Power in Chip


» Example from a Sun 8-core processor ("Niagra2")



Copyright © 2011 Pearson Education Inc. Publishing as Pearson Addison-Wesley
 
# The Death of Moore's Law ☹️

Power and Heat Problems Led to Multiple Cores and Prevent Further Improvements in Speed



Original data collected and plotted by M. Horowitz, F. Labonte, O. Shacham, K. Olukotun, L. Hammond and C. Batten  
Dotted line extrapolations by C. Moore  
Source: Chuck Moore, Data Processing in Exascale-Class Systems, April 27, 2011. Salishan Conference on High Speed Computing