

Digital Integrated Circuit Design  
CMPE 530/630

---

# Sequential Circuit Design

Dr. Cory Merkel



# Outline

- » Sequencing
- » Sequencing Element Design
- » Max and Min-Delay
- » Clock Skew
- » Time Borrowing
- » Two-Phase Clocking


# Sequencing

## » Combinational logic


- Output depends on current inputs
 
## » Sequential logic

- Output depends on current and previous inputs
- Requires separating previous, current, future
- Called *state* or *tokens*
- Ex: FSM, pipeline



Finite State Machine

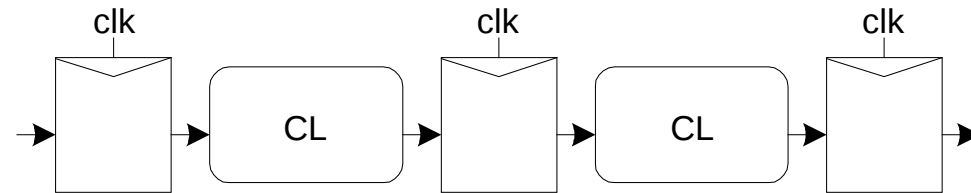

Pipeline

## Sequencing Cont.

- » If tokens moved through pipeline at constant speed, no sequencing elements would be necessary
- » Ex: fiber-optic cable
  - Light pulses (tokens) are sent down cable
  - Next pulse sent before first reaches end of cable
  - No need for hardware to separate pulses
  - But *dispersion* sets min time between pulses
- » This is called *wave pipelining* in circuits
- » In most circuits, dispersion is high
  - Delay fast tokens so they don't catch slow ones.

## Sequencing Overhead

- » Use flip-flops to delay fast tokens so they move through exactly one stage each cycle.
- » Inevitably adds some delay to the slow tokens
- » Makes circuit slower than just the logic delay
  - Called sequencing overhead
- » Some people call this clocking overhead
  - But it applies to asynchronous circuits too
  - Inevitable side effect of maintaining sequence

# Sequencing Elements

## » Latch: Level sensitive


- a.k.a. transparent latch, D latch

## » Flip-flop: edge triggered

- A.k.a. master-slave flip-flop, D flip-flop, D register

## » Timing Diagrams

- Transparent
- Opaque
- Edge-trigger






 


# Timing Diagrams

- Key parameters in sequential elements:

Contamination and Propagation Delays

|             |                               |
|-------------|-------------------------------|
| $t_{pd}$    | Logic Prop. Delay             |
| $t_{cd}$    | Logic Cont. Delay             |
| $t_{pcq}$   | Latch/Flop Clk->Q Prop. Delay |
| $t_{ccq}$   | Latch/Flop Clk->Q Cont. Delay |
| $t_{pdq}$   | Latch D->Q Prop. Delay        |
| $t_{cdq}$   | Latch D->Q Cont. Delay        |
| $t_{setup}$ | Latch/Flop Setup Time         |
| $t_{hold}$  | Latch/Flop Hold Time          |

      

# Latch Design


## » Pass Transistor Latch

### » Pros

- + Tiny
- + Low clock load
 
### » Cons


- $V_t$  drop
- Nonrestoring
- Backdriving
  - Output drives input
- Output noise sensitivity
- Dynamic – Output floats when latch is opaque
- Diffusion input
  - Noise at  $D$  could cause transistor to turn on unintentionally
- Subthreshold leakage – How long does state last?



Used in 1970's

# Latch Design

## » Pass Transistor Latch Delays:

 

$$t_{pcq} \approx t_{ccq} \approx R_{\phi}C + R_D C + (R_D + R)C$$

$$t_{pdq} \approx R_D C + (R_D + R)C$$

$$t_{setup} \approx K t_{pdq}, \text{ e.g. } K = 3 \text{ gets us to 95\% of final value}$$


$$t_{hold} \approx R_{\phi}C - t_{pdq}$$

\*Recall that there is a factor of  $\ln 2$  in these equations.

# Latch Design
 
## » Transmission gate

- + No  $V_t$  drop
- Requires inverted clock



$$\begin{aligned}
 t_{pcq} &\approx t_{ccq} \\
 &\approx R_\phi 4C + 5RC + R_D 3C + (R_D + R/2)3C \\
 t_{pdq} &\approx R_D 3C + (R_D + R/2)3C
 \end{aligned}$$


$$t_{setup} \approx K t_{pdq}, \text{ e.g. } K = 3 \text{ gets us to 95\% of final value}$$

$$t_{hold} \approx R_\phi 4C + 5RC - t_{pdq}$$

# Latch Design
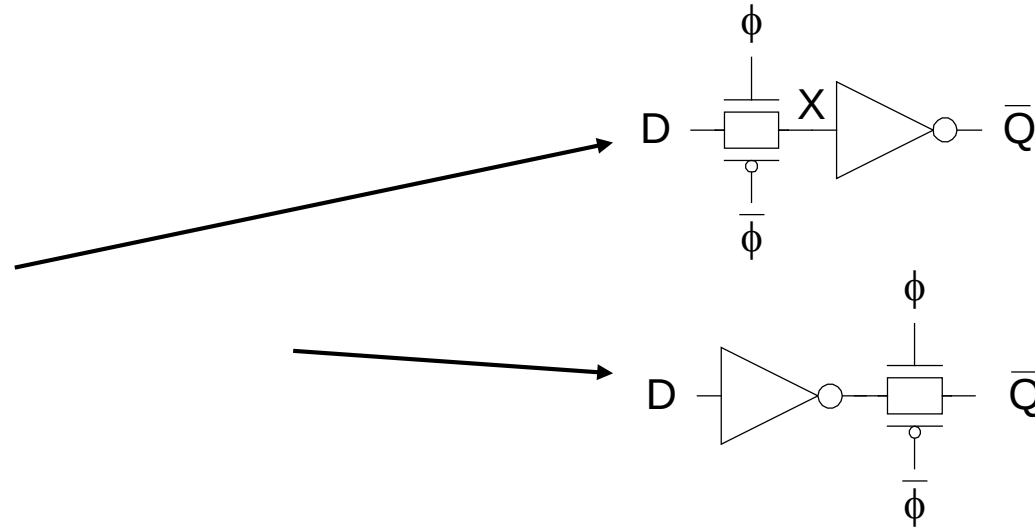
## » Inverting buffer


- + Restoring
- + No backdriving
- + Fixes either
  - Diffusion input
  - Or output noise sensitivity
- Inverted output



# Latch Design

 
## » Clocked CMOS (C<sup>2</sup>MOS):

- + No diffusion input
- + Small
- Dynamic


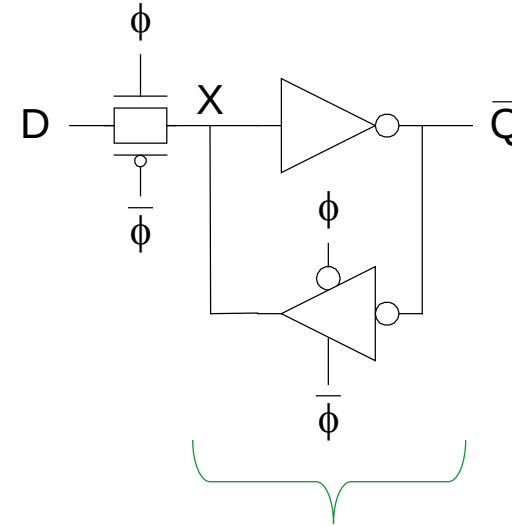
# Latch Design

- » Tristate feedback
  - + Static
    - Backdriving risk
- » Static latches are now essential because of leakage




**Does this need to be tri-state? Why?**

# Latch Design

 
## » Buffered input

- + Fixes diffusion input
- + Noninverting
- Noise at output could change state


 
# Latch Design


- » Buffered output
  - + No backdriving
- » Widely used in standard cells
  - + Very robust (most important)
  - Rather large
  - Rather slow (1.5 – 2 FO<sub>4</sub> delays)
  - High clock loading




# Latch Design
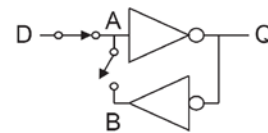
## » Metastability


- There are unstable fixed (metastable) points in the latch's voltage space
- Any small disturbance will cause the latch to move from the metastable point to a stable value




(a)

 

(b)

 


(c)

 

(d)
 
# Latch Design

- » Consider a critical delay  $t_m$  between  $D$  and the latch input
- If  $D$  changes  $\approx t_m$  before  $\phi$ , then the latch will be near a metastable state
  - The closer  $D$  changes to the critical point, the longer the output will take to settle



## Latch Design


- » The latch's behavior near the metastable point  $V_m$  can be modeled using a small signal model:
- » Initial voltage on the latch input when it becomes opaque:

$$A(0) = V_m + a(0)$$

where  $a$  is a small signal offset

- » Then,
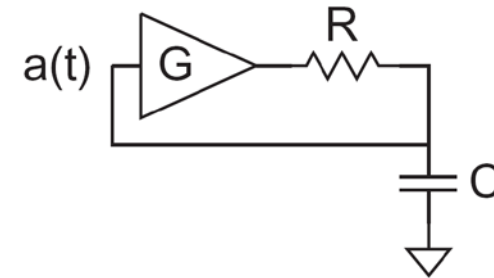
$$\frac{Ga(t) - a(t)}{R} = C \frac{da(t)}{dt}$$



or,

$$a(t) = a(0)e^{t/\tau_s}, \quad \tau_s \equiv \frac{RC}{G - 1}$$


- » Now, define  $\Delta V$  to be the voltage deviation required at the input node for the latch's state to be considered valid:

$$t_{DQ} = \tau_s [\ln \Delta V - \ln a(0)]$$

# Latch Design

 
## » Datapath latch

- + smaller
- + faster
- unbuffered input


 
# Flip-Flop Design


- » Flip-flop is built as pair of back-to-back latches



# Flip-Flop Design
 
## » Setup Time


- Setup time is the time it takes for  $D$  to be reflected in the master latch:



# Flip-Flop Design
 
## » Hold Time:


- Hold time is the difference between the time it takes  $D$  to be reflected at latch input (after the TG) and the time it takes for the TG to turn off after clock edge




# Enable

- » Enable: ignore clock when  $en = 0$ 
  - Mux: increase latch D-Q delay
  - Clock Gating: increase en setup time, skew





Symbol

 

Multiplexer Design

 


Clock Gating Design

   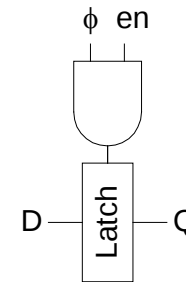

 
# Reset

- » Force output low when reset asserted
- » Synchronous vs. asynchronous




 
## Set / Reset

- » Set forces output high when enabled
- » Flip-flop with asynchronous set and reset



  
# Characterizing Sequencing Elements

- » Sequencing elements such as flip flops can be characterized via simulation
- » Example:
  - Deriving the setup time as the  $t_{DC}$  that yields the minimum  $t_{DQ}$



 
# Sequencing Methods

- » Flip-flops
- » 2-Phase Latches
- » Pulsed Latches



 
# Max-Delay: Flip-Flops

$$t_{pd} \leq T_c - \underbrace{(t_{\text{setup}} + t_{pcq})}_{\text{sequencing overhead}}$$



 
# Max Delay: 2-Phase Latches

$$t_{pd} = t_{pd1} + t_{pd2} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$



 
# Max Delay: Pulsed Latches

$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{setup} - t_{pw})}_{\text{sequencing overhead}}$$


 
# Min-Delay: Flip-Flops

$$t_{cd} \geq t_{\text{hold}} - t_{ccq}$$




## Min-Delay: 2-Phase Latches

$$t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}}$$

Hold time reduced by nonoverlap

Paradox: hold applies twice each cycle, vs. only once for flops.


But a flop is made of two latches!

 

# Min-Delay: Pulsed Latches

$$t_{cd} \geq t_{\text{hold}} - t_{ccq} + t_{pw}$$

Hold time increased by pulse width

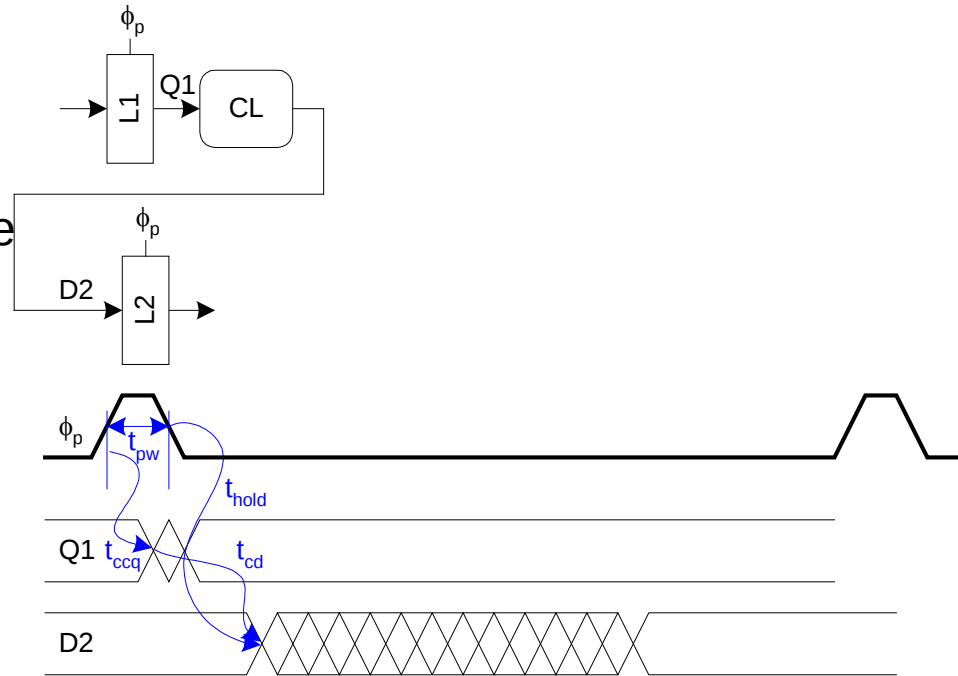

# Time Borrowing


## » In a flop-based system:

- Data launches on one rising edge
- Must setup before next rising edge
- If it arrives late, system fails
- If it arrives early, time is wasted
- Flops have hard edges

## » In a latch-based system

- Data can pass through latch while transparent
- Long cycle of logic can borrow time into next
- As long as each loop completes in one cycle

# Time Borrowing Example

 


# How Much Borrowing?

## 2-Phase Latches

$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}})$$
 
## Pulsed Latches

$$t_{\text{borrow}} \leq t_{pw} - t_{\text{setup}}$$




# Clock Skew

- » We have assumed zero clock skew
- » Clocks really have uncertainty in arrival time
  - Decreases maximum propagation delay
  - Increases minimum contamination delay
  - Decreases time borrowing
 
# Skew: Flip-Flops

$$t_{pd} \leq T_c - \underbrace{(t_{pcq} + t_{setup} + t_{skew})}_{\text{sequencing overhead}}$$

$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$



# Skew: Latches

## 2-Phase Latches

$$t_{pd} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$

$$t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}} + t_{\text{skew}}$$


$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}} + t_{\text{skew}})$$

## Pulsed Latches

$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{\text{setup}} - t_{pw} + t_{\text{skew}})}_{\text{sequencing overhead}}$$

$$t_{cd} \geq t_{\text{hold}} + t_{pw} - t_{ccq} + t_{\text{skew}}$$
 
$$t_{\text{borrow}} \leq t_{pw} - (t_{\text{setup}} + t_{\text{skew}})$$




## Two-Phase Clocking

- » If setup times are violated, reduce clock speed
- » If hold times are violated, chip fails at any speed
- » In this class, working chips are most important
  - No tools to analyze clock skew
- » An easy way to guarantee hold times is to use 2-phase latches with big nonoverlap times
- » Call these clocks  $\phi_1$ ,  $\phi_2$  (ph1, ph2)
 
# Safe Flip-Flop


- » Past years used flip-flop with nonoverlapping clocks
  - Slow – nonoverlap adds to setup time
  - But no hold times
- » In industry, use a better timing analyzer
  - Add buffers to slow signals if hold time is at risk


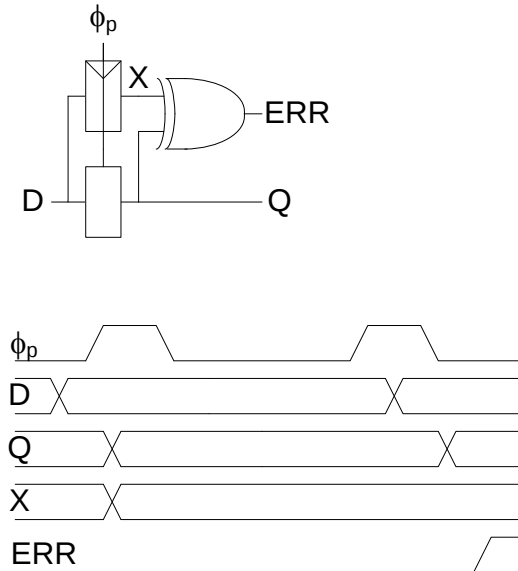
# Adaptive Sequencing

- Designers include timing margin

- Voltage
- Temperature
- Process variation
- Data dependency
- Tool inaccuracies



- Alternative: run faster and check for near failures

- Idea introduced as "Razor"
  - Increase frequency until at the verge of error
  - Can reduce cycle time by ~30%

# Summary

## » Flip-Flops:

- Very easy to use, supported by all tools

## » 2-Phase Transparent Latches:

- Lots of skew tolerance and time borrowing

## » Pulsed Latches:

- Fast, some skew tol & borrow, hold time risk

|                                     | Sequencing overhead<br>( $T_c - t_{pd}$ )                | Minimum logic delay<br>$t_{cd}$                                        | Time borrowing<br>$t_{borrow}$                            |
|-------------------------------------|----------------------------------------------------------|------------------------------------------------------------------------|-----------------------------------------------------------|
| Flip-Flops                          | $t_{pcq} + t_{setup} + t_{skew}$                         | $t_{hold} - t_{ccq} + t_{skew}$                                        | 0                                                         |
| Two-Phase<br>Transparent<br>Latches | $2t_{pdq}$                                               | $t_{hold} - t_{ccq} - t_{nonoverlap} + t_{skew}$<br>in each half-cycle | $\frac{T_c}{2} - (t_{setup} + t_{nonoverlap} + t_{skew})$ |
| Pulsed<br>Latches                   | $\max(t_{pdq}, t_{pcq} + t_{setup} - t_{pw} + t_{skew})$ | $t_{hold} - t_{ccq} + t_{pw} + t_{skew}$                               | $t_{pw} - (t_{setup} + t_{skew})$                         |